

Capacitors MS2

Question Number	Answer	Mark
1(a)(i)	<p>The idea that electrons move from one plate to the other plate through the external circuit (1)</p> <p>When fully charged there is no movement of electrons Or As capacitor charges, rate of flow of electrons decreases Or (when fully charged) p.d. across the plates/capacitor is equal (and opposite) to the supply p.d. Or (when fully charged) equal and opposite charge/electrons on each plate (1)</p>	2
1(a)(ii)	<p>Use of $W = \frac{1}{2} CV^2$ Or use of $Q=CV$ and $W=\frac{1}{2}QV$ (1)</p> <p>$W = 0.34 \text{ J}$ (1)</p> <p><u>Example of calculation</u></p> <p>$W = 0.5 \times 4700 \times 10^{-6} \text{ F} \times (12 \text{ V})^2 = 0.34 \text{ J}$</p>	2
1(b)(i)	<p>Current decreases (over time) (1)</p> <p>Exponentially (1)</p> <p>(a graph of I/t with I decreasing can score MP1. Must be indicated as exponential for MP2)</p>	2
1(b)(ii)	<p>Use of $V = V_0 e^{-t/RC}$ Or see $\ln(V/V_0) = -t/RC$ (1)</p> <p>Use $V = 1.2 \text{ (V)}$ and $V_0 = 12 \text{ (V)}$ Or use $\frac{V}{V_0} = 0.1$ (1)</p> <p>$R = 2300 \ \Omega$ (1)</p> <p><u>Example of calculation</u></p> <p>$V = V_0 e^{-t/RC}$</p> <p>$\ln\left(\frac{V}{V_0}\right) = \frac{-t}{RC}$</p> <p>$\ln(0.1) = \frac{-25 \text{ s}}{R \times 4700 \times 10^{-6} \text{ F}}$</p> <p>$R = \frac{-25 \text{ s}}{\ln 0.1 \times 4700 \times 10^{-6} \text{ F}}$</p> <p>$R = 2300 \ \Omega$</p>	3
Total for question 1		9

Question Number	Answer	Mark
2(a)(i)	<p>Use of $I = I_0 / e$ (I_0 from 2.35 mA to 2.4 mA) to find time constant (1)</p> <p>Or intercept with t axis using initial tangent to find time constant (range 125 s to 135 s)</p> <p>Use of time constant = RC (1)</p> <p>$C = 0.015$ (F) to 0.017 (F) (1)</p> <p>Or</p> <p>Attempts a pair of readings of I and t from graph (1)</p> <p>Use of $I = I_0 e^{-t/RC}$ (1)</p> <p>$C = 0.015$ (F) to 0.017 (F) (1)</p> <p>Or</p> <p>Attempts to obtain 'half-life' from graph (1)</p> <p>Use of $t_{1/2} = RC \ln 2$ (1)</p> <p>$C = 0.015$ (F) to 0.017 (F) (1)</p> <p><u>Example of calculation</u></p> <p>$131 \text{ s} = 8200 \Omega \times C$</p> <p>$C = 1.60 \times 10^{-2} \text{ F}$</p>	3
2(a)(ii)	<p>Use of $V = IR$ for initial p.d. using initial current (1)</p> <p>Use of $C = Q/V$ ecf from (i) (1)</p> <p>$Q = 0.32 \text{ C}$ (1)</p> <p><u>Example of calculation</u></p> <p>$V = 0.0024 \text{ A} \times 8200 \Omega = 19.7 \text{ V}$</p> <p>$\Delta Q = 1.60 \times 10^{-2} \text{ F} \times 19.7 \text{ V} = 0.316 \text{ C}$</p>	3
2(a)(iii)	<p>Use of suitable equation, e.g. $W = \frac{1}{2} QV$ ecf from (i) and (ii) (1)</p> <p>$W = 3.1 \text{ J}$ (1)</p> <p><u>Example of calculation</u></p> <p>$W = \frac{1}{2} \times 0.316 \text{ C} \times 19.7 \text{ V}$</p> <p>$W = 3.08 \text{ J}$</p>	2
2(b)	<p>Use of $V = V_0 e^{-\frac{t}{RC}}$ (1)</p> <p>Correct use of 15% (1)</p> <p>$R = 240 \text{ k}\Omega$ (1)</p> <p><u>Example of calculation</u></p> <p>$0.15 V_0 = V_0 e^{-\frac{t}{RC}}$</p> <p>$\ln 0.15 + \ln V_0 = \ln V_0 - \frac{t}{RC}$</p> <p>$\ln 0.15 = \frac{-0.10 \text{ s}}{R \times 470 \times 10^{-6} \text{ F}}$</p> <p>$R = 2.36 \times 10^5 \Omega$</p>	3
	Total for question 2	11

Question Number	Answer	Mark
3(a)	<p>Method marks only</p> <p>Use of $Q=CV$ with $V=16\text{ V}$ (1)</p> <p>Max value of $C = 12000\ (\mu\text{F})$ (1)</p> <p>μF means 10^{-6} conversion of μF to F (1)</p> <p><u>Example of calculation</u></p> <p>$C_{\text{max}} = 1.20 \times 10000 = 12000\ \text{F}$</p> <p>$C_{\text{max}} = 12000\ \text{F} \times 16\ \text{V}$</p> <p>$Q_{\text{max}} = 0.192\ \text{C}$</p>	3
3(b)	<p>Either use of $\frac{1}{2} QV$ or $\frac{1}{2} CV^2$ (1)</p> <p>Energy = 1.5 J (1)</p> <p><u>Example of calculation</u></p> <p>$W = \frac{1}{2} 0.192\ \text{C} \times 16\ \text{V}$</p> <p>Energy = 1.54 J</p>	2
Total for question 3		5

Revisionmadesimple.com

Question Number	Answer	Mark
4(a)(i)	Use of $t=RC$ (1)	3
	Use of $T=1/f$ Or $f = 1/t$ (1)	
	Comparison of 2.2×10^{-4} (s) \ll 2.5×10^{-3} (s) Or comparison of 400 (Hz) \ll 4500 (Hz) Or reference to nRC (needed for complete discharge) where $n = 3 - 11$ Or $e^{-T/t}$ is a very small value (1)	
4(a)(ii)	See $C = Q/V$ Or $Q = CV$ (1) See $Q = It$ (1) See $t = 1/f$ Or $f = 1/t$ (1) (Answers based on $t = RC$ and $V = IR$ scores 0)	3
4(a)(iii)	sub in $C = I/fV$ (1) $C = 2.7 \mu\text{F}$ (1) <u>Example of calculation</u> $C = 5.4 \times 10^{-3} \text{ A} / (400 \text{ s}^{-1} \times 5.0 \text{ V})$ $C = 2.7 \mu\text{F}$	2
4(a)(iv)	$2.2 + 30\% = 2.9 (\mu\text{F})$ Or shows that $2.7 (\mu\text{F})$ is +22% of $2.2 (\mu\text{F})$ (1) Within tolerance / consistent (1) (2nd mark can only be awarded following an attempt at either of the above calculations) If candidates make an error in (iii) allow full ecf with a valid comment based on their values.	2
4(b)	Use of $\frac{1}{2} CV^2$ (1) $W = 3.4 \times 10^{-5} \text{ J}$ (1) (allow ecf from (iii) or use of $2.2 \mu\text{F} \rightarrow 2.75 \times 10^{-5} \text{ J}$) <u>Example of calculation</u> $W = \frac{1}{2} 2.7 \mu\text{F} \times (5.0 \text{ V})^2$ $W = 3.4 \times 10^{-5} \text{ J}$	2
Total for question 4		12

Question Number	Answer	Mark
5(a)(i)	(Capacitor) discharges Or loses charge Or p.d. across capacitor falls The idea that the discharge is not instantaneous [e.g., gradually, exponentially, over time]	(1) (1) 2
5(a)(ii)	Decay curve starting on y - axis but not touching x -axis. Initial current 2 mA Time axis labelled to indicate ($t_{1/2} =$) 0.03 s Or Time axis labelled to indicate ($RC =$) 0.04 s Or Time axis labelled to indicate ($5RC =$) 0.2s	(1) (1) (1) 3
5(a)(iii)	Initially large current Or capacitor charges up Over a very short time Or happens instantaneously Because resistance is not in the charging circuit Or because $R = 0$	(1) (1) (1) 3
5(b)	Use of $V = V_0 e^{-t/RC}$ with $V_0 = 20V$ Correct conversion of both units $V = 0.13 V$ <u>Example of calculation</u> $V = V_0 e^{-t/RC}$ $V = 20 V e^{-0.20 / 10 \times 10^3 \times 4 \times 10^{-6}}$ $V = 0.13 V$	(1) (1) (1) 3
5(c)	Use of $W = CV^2/2$ Use of $KE = mv^2/2$ $E_C/E_K = 0.023$ <u>Example of calculation</u> $E_C = CV^2/2 = 2600 F \times (2.5 V)^2 / 2 = 8125 J$ $E_K = mv^2/2 = 800 kg \times (30 m s^{-1})^2 / 2 = 360 000 J$ $E_C/E_K = 0.023$	(1) (1) (1) 3
	Total for question 5	14

Question Number	Answer	Mark
6(a)	Use of $C=Q/V$ (1) $V=15\text{ V}$ (1) Use of $W=QV/2$ Or $W=CV^2/2$ Or $W=Q^2/2C$ (1) $W=2.5 \times 10^{-5}\text{ J}$ (1) (candidates who use $6.6 \times 10^{-6}\text{ C}$ can only score MP1 and MP3) <u>Example of calculation</u> $V=Q/C=3.3 \times 10^{-6}\text{ C} / 220 \times 10^{-9}\text{ F}$ $V=15\text{ V}$ $W=QV/2=(3.3 \times 10^{-6}\text{ C} \times 15\text{ V})/2$ $W=2.5 \times 10^{-5}\text{ J}$	4
6(b)	$Q=0.2 Q_0$ Or $Q=6.6 \times 10^{-7}\text{ C}$ (1) Use of $Q=Q_0 e^{-t/RC}$ (1) $t=7.1\text{ s}$ (1) (candidates who use $Q=0.8 Q_0$ can only score MP2) <u>Example of calculation</u> $Q=0.2 Q_0$ $Q=Q_0 e^{-t/RC}$ $0.2 Q_0=Q_0 e^{-t/RC}$ $\ln(0.2)=-t/(20 \times 10^6\ \Omega \times 220 \times 10^{-9}\text{ F})$ $t=7.1\text{ s}$	3
6(c)	Either refers to $W=Q^2/2C$ Or $W \propto Q^2$ (1) If Q halves, $W \rightarrow Q^2/8C$ Or halving Q quarters W (1) (Since W becomes a quarter in the time for Q to half) it takes less time for the energy to halve than the charge to halve. (dependent mark on either MP1 or MP2) (1) Or Refers to $W=QV/2$ (1) Q and V both decrease over time (1) W will decrease faster so takes less time to half in value. (dependent mark on either MP1 or MP2) (1)	3
6(d)	Synchronous readings Or data logger records readings at exact time (1) Or voltmeter and stop watch need 2 people and data logger only one (1) More readings can be taken in a shorter time Or higher sampling rate (1) (treat as neutral any reference to graph plotting automatically, human reaction time or accuracy)	2
Total for question 6		12

Question Number	Answer	Mark
8*(a)	<p>(QWC – Work must be clear and organised in a logical manner using technical wording where appropriate)</p> <p>Between the plates there is a force (references to repulsion and attraction are not sufficient) (1)</p> <p>Gives a downward acceleration Or accelerates towards the negative plate (1)</p> <p>Constant horizontal velocity Or no forces act horizontally (1)</p> <p>Outside the plates no (electric) field /force acts Or Outside the plates speed so large that gravitational effect negligible (1)</p>	4
8(b)(i)	<p>Magnetic force = electric force Or $Eq = Bqv$ (1)</p> <p>Forces must act in opposite directions Or resultant force is zero. Or (magnetic) field into page (1)</p> <p>(do not credit if forces stated as being perpendicular to each other)</p>	2
8(b)(ii)	<p>Use of $E = V/d$ (1)</p> <p>Evidence of equating two forces $Bqv = Eq$ (award if you see $Bv = E$) (1)</p> <p>Both unit conversions correct. (1)</p> <p>$B = 5.1 \times 10^{-3} \text{ T}$ (1)</p> <p>(There is no credit for alternative methods where assumptions have to be made about value of charge and /or mass)</p> <p><u>Example of calculation</u> $E = V/d$ $Bqv = Eq$ $B = E/v = V/dv$ $B = 60 \text{ V} / (4.5 \times 10^{-2} \text{ m} \times 260 \times 10^3 \text{ m s}^{-1})$ $B = 5.1 \times 10^{-3} \text{ T}$</p>	4
8(c)	<p>Upward path (not downwards) Or magnetic path is arc of a circle (1)</p> <p>Magnetic force changes direction as ions path changes Or magnetic force perpendicular to path/velocity of ion. (1)</p> <p>Electric force constant direction Or electric force always acts downwards. Or electric path is parabolic (1)</p>	3
	Total for Question 8	13